

22320

22223

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
 - (8) Preferably, write the answers in sequential order.

Marks

- 1. Attempt any FIVE of the following: **10****
- a) State the base of following number system:
Decimal, binary, octal, hexadecimal
 - b) Define counter.
 - c) Give any two applications of comparator.
 - d) Draw the symbol of D flipflop and write its truth table.
 - e) Name the types of RAM.
 - f) Define and draw logic symbol of demultiplexer.
 - g) List the basic types of shift register.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Convert the given binary into decimal, octal, hexadecimal and gray code:
(10110101)₂
 - b) Draw the block diagram of BCD to 7 segment decoder using IC 7447. Write truth table of it.
 - c) Define PLA. Draw its block diagram.
 - d) Implement full adder using two half adder.
- 3. Attempt any THREE of the following:** **12**
- a) Draw the OR gate and NOR gate using NAND gate only.
 - b) Compare TTL, ECL and CMOS logic families. (any four points)
 - c) Draw 4 bit twisted ring counter and explain working with truth table and waveforms.
 - d) A combinational circuit is defined as $F_1 = \sum m(3, 5, 7)$ and $F_2 = \sum m(4, 5, 7)$. Implement the circuit with a PLA having 3 inputs, 3 product terms and 2 outputs.
- 4. Attempt any THREE of the following:** **12**
- a) Define following terms :
 - i) Fan-in
 - ii) Fan-out
 - iii) Power dissipation
 - iv) Noise margin
 - b) Draw the block diagram of digital comparator IC 7485 and explain with the help of truth table.
 - c) Design 32 : 1 multiplexer using 8 : 1 multiplexer.
 - d) Explain the working of master slave JK flipflop with truth table and logic diagram.
 - e) Write applications of ADC and DAC.

- 5. Attempt any TWO of the following:** **12**
- a) Design mod-6 counter using IC 7490 and explain its design with working.
- b) Explain classification of memories. What is flash memory?
- c) i) State the rules of BCD addition. (2)
ii) Perform BCD addition of : (4)
 $(972)_{10} + (348)_{10}$
- 6. Attempt any TWO of the following:** **12**
- a) Design synchronous decade counter using D' flipflop.
- b) i) Minimize the following expression using K-map. (4)
 $Y = \sum m(0, 2, 5, 7, 8, 10, 13, 15)$
ii) Realize the minimized expression using basic gates. (2)
- c) Reduce following boolean expressions using boolean laws.
- i) $Y = A\bar{B} + \bar{A}B + AB + \bar{A}\bar{B}$ (2)
- ii) $Y = A\bar{B}C + \bar{A}BC + ABC$ (2)
- iii) $Y = ABC + \bar{A}BC + ABC$ (2)
-